



Be the best that we can be.

EBJ Knowledge Organiser Science Year 6









Summer 1

Energy: Circuits, batteries and switches




Drawing Circuits

A **component** is a device in an electrical circuit. Symbols are often used to represent the components so they are easier to draw and easily recognised.

 Cell - a single unit of power.	 Battery - more than one cell.	 Wire - connects components in a circuit.	 Open switch - breaks a circuit.
 Closed switch - completes a circuit.	 Bulb - gives out light.	 Buzzer - makes sound.	 Motor - moves.

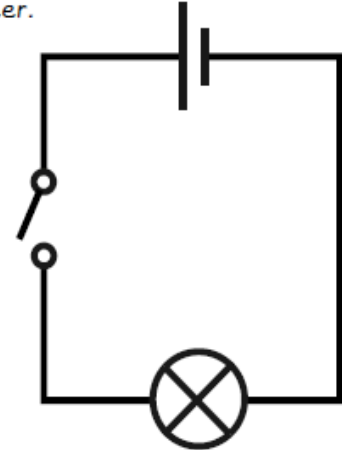A **circuit diagram** is a simple line drawing that represents how the components in an appliance join together.



A complete circuit must have a **power supply**, a **complete loop** and at least one **component**.


Key vocabulary

Some of our investigations

current	A measure of how much electrical charge flows through a circuit.
resistance	Something that slows the flow of current/electrical charge in a circuit.
voltage	The measure of how much energy is carried by electrical charge; the 'push' from the power source.

Investigating bulb brightness and resistance

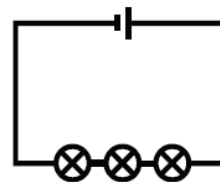The more bulbs, the dimmer their brightness.




Or the more buzzers, the quieter the sound.

- The more components added to a circuit, the greater the resistance.
- This makes it harder for the current (charge) to flow.
- Less energy is transferred so the bulbs are dimmer.

Electrical Conductors

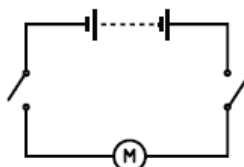
If more than one switch is used in a circuit, both need to be closed for it to work. These are often used to keep people safe with dangerous appliances.



Switches need materials that are **electrical conductors** to complete the circuit.

Investigating bulb brightness and voltage

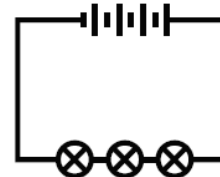The more cells, the higher the voltage and the brighter the bulbs.



Or the more cells, the louder the buzzer.

- The more cells added, the higher the voltage.
- The higher the voltage, the more 'push' there is of the current.
- More energy is transferred so the bulbs are brighter.